

Operational Amplifiers: Part 1

The Ideal Feedback Amplifier

by

Tim J. Sobering

Analog Design Engineer
& Op Amp Addict

Housekeeping (I)

Gain


- **Transfer function** from input to output of a circuit, amplifier, network
- In simplest form, a ratio (Volt/Volt, Volt/Amp, Watt/Watt)
- Often complex, having magnitude and phase
- Voltage Gain, Power Gain, Current Gain, etc.

“Gain” can be less than one, positive, or negative

- The “gain” of a resistor divider is $\frac{V_{OUT}}{V_{IN}} = \frac{R_2}{R_1 + R_2}$
- A gain less than one is an “Attenuator”
- Negative gain means a “phase shift” (180°)
- It is often a complex number (magnitude and phase)

Often linear, but can be nonlinear

- Log or anti-log amplifier

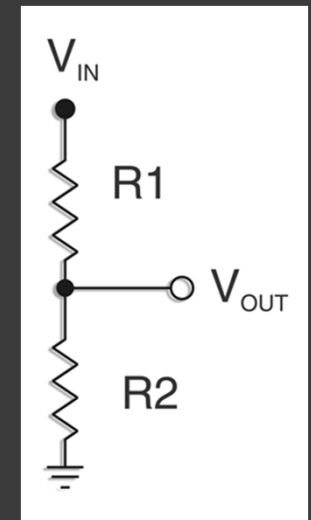

Housekeeping (II)

⦿ Decibel (dB)

- Logarithmic unit for the ratio between two values
- A factor of 10 change in power is 10 dB; 100 → 20 dB

$$\text{Power Gain}(dB) = 10 \log_{10} \left(\frac{\text{Power}_1}{\text{Power}_0} \right)$$

- A factor of 10 change in power is “equivalent” to a factor of 100 change in voltage and so is 20 dB (i.e. power is proportional to V^2)

$$\text{Voltage Gain}(dB) = 20 \log_{10} \left(\frac{\text{Voltage}_1}{\text{Voltage}_0} \right)$$

⦿ dB can be a relative to a reference level

- dBm – power relative to 1 mW
- dBV – voltage relative to 1V (dBmV, dB μ V)
- dBu – voltage relative to 0.775V
- dB SPL – sound pressure level relative to 20 micropascals

And one last thing...


“Analog is dead”

– (semi) Anonymous

And one last thing...

“Analog is dead”

– (semi) Anonymous

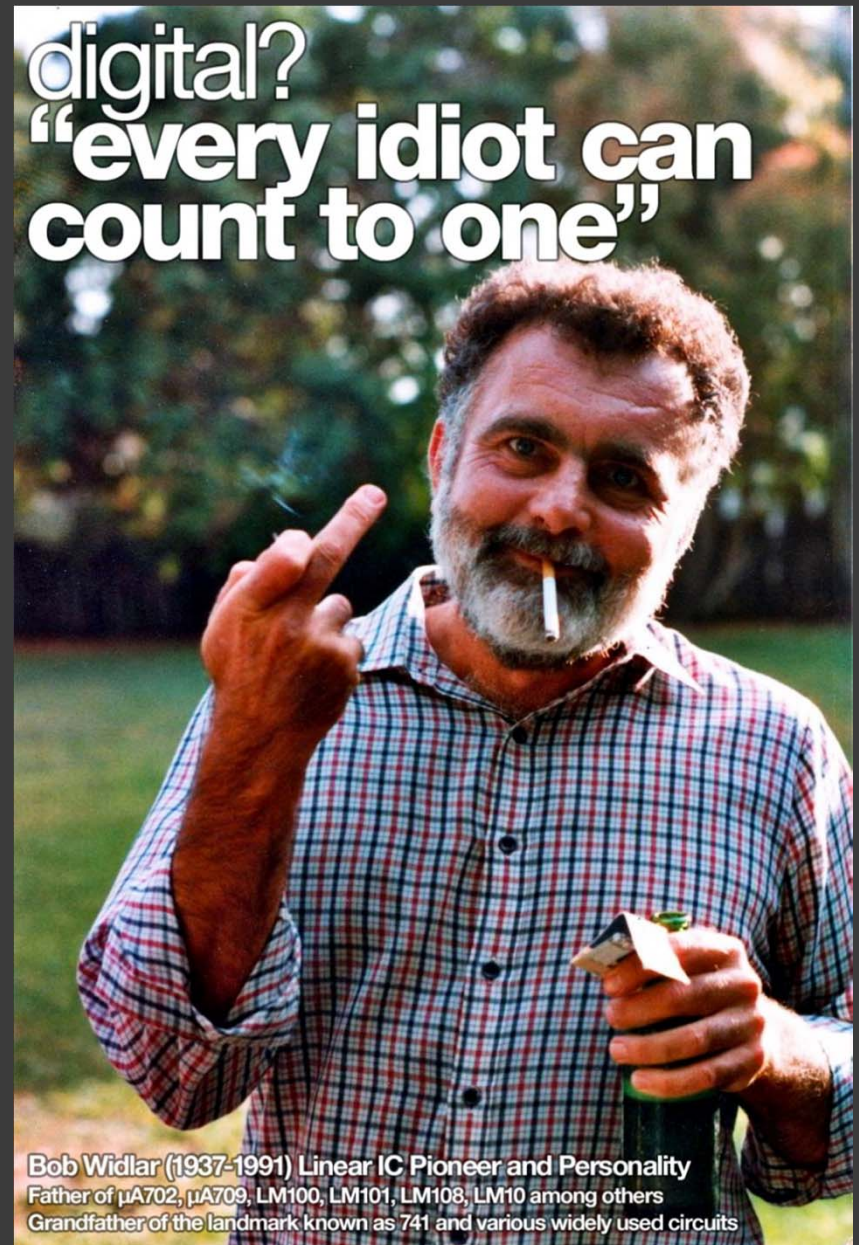

A little history...


- ◎ Modern Op Amps owe their existence to Edison's light bulb
 - “Fleming diode” – J.A. Fleming added a plate electrode to Edison's filament lamp to create a simple rectifier
 - “Audion” – Lee De Forest added a control grid between the filament and the plate and obtained “gain” – the first amplifier
- ◎ This formed the foundation for electronic (tube) amplifiers, but we needed a few inventions before we had an Op Amp
- ◎ Early amplifiers has a lot of problems
 - Amplifiers were highly customized for each application
 - Amplifier characteristics drifted and depended on source and load
 - The characteristics of the source and load changed with time and temperature

This was called the “telephone amplifier problem”

- ⦿ Amplifiers in telephone repeater amplifiers were problematic
 - Difficult to stabilize
 - Stage gain variations
 - Lots of distortion
- ⦿ Simply put, the sound quality was terrible
 - Echoes
 - Variations in volume
 - Pops, whistles, and other fun noises
 - Long distance transmission was a challenge
- ⦿ *Imagine only being able to design a car to operate with specific road conditions and at a specific speed*
 - *Yet it still shook and shimmied*
 - *It didn't work at all on a different road*
 - *Big problem!*

The solution came to Harold S. Black while riding the ferry to work at Bell Labs

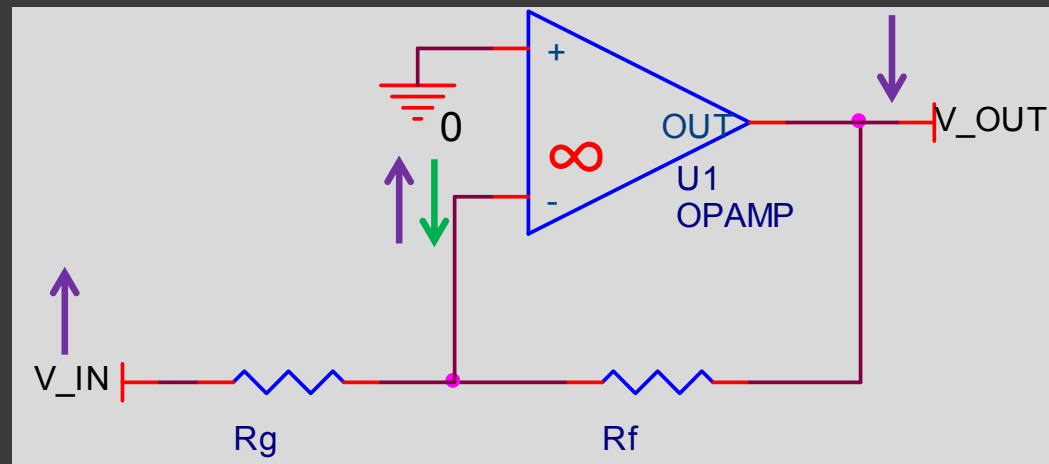
- Black conceived the “negative feedback” amplifier (1934)
 - All Op Amp circuits (that amplify) are based on the principal of negative feedback



- *With negative feedback, the amplifier output will (try to) force the input voltage difference to zero*
 - This results in some very unique and beneficial properties
- Experienced engineers resisted Black's discovery
 - “Throwing away” gain seemed counterintuitive


Some more definitions are needed...

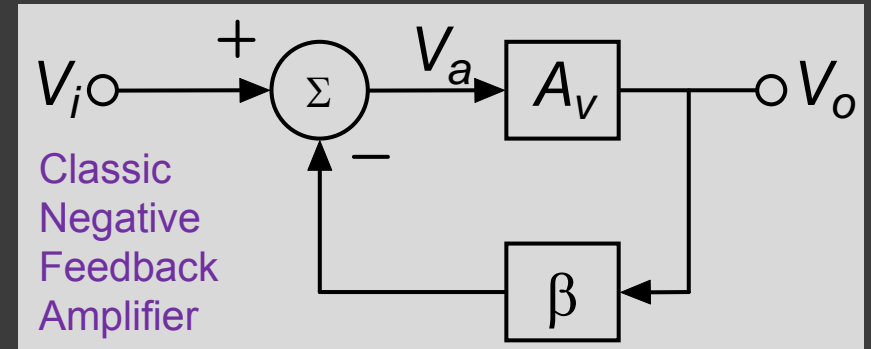- ◎ A_v – Open Loop Gain
 - Gain without feedback
 - Ideally $A_v \rightarrow \infty$
 - Some use A , A_o , A_{ol} , etc.



- ◎ $A_{cl} = V_o / V_i$ – Closed Loop Gain
 - Gain with Negative Feedback loop closed
- ◎ β – Feedback Factor
 - The portion of output that is “fed back” to the input (usually ≤ 1)
- ◎ $A_v \beta$ – Loop Gain
 - Gain around the feedback loop (spoiler alert...this is the important one)

Analysis is easy...

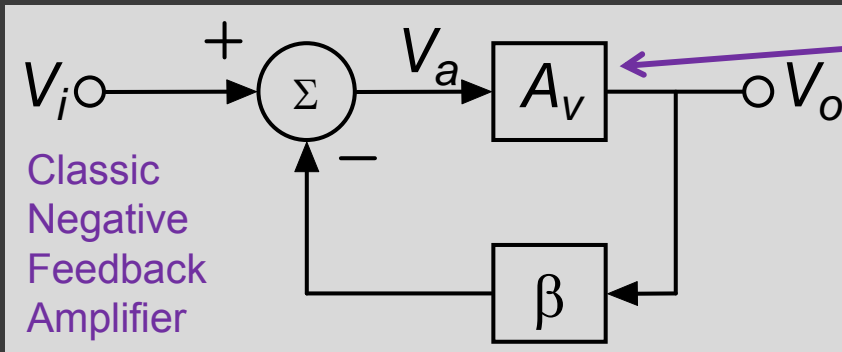

That's the Op Amp...

A high gain, differential input, amplifier

- A_{cl} depends (primarily) on β – the feedback network design
- Changes in A_v have little effect on A_{cl} (and bandwidth)
- $A_v \beta$ is the gain Black “threw away”


$$V_o = A_v(V_i - \beta V_o)$$

$$V_o(1 + A_v\beta) = A_v V_i$$

$$\frac{V_o}{V_i} = \frac{A_v}{1 + A_v\beta} = \frac{1}{\frac{1}{A_v} + \beta}$$

Let $A_v \rightarrow \infty$ (*ideal assumption*)
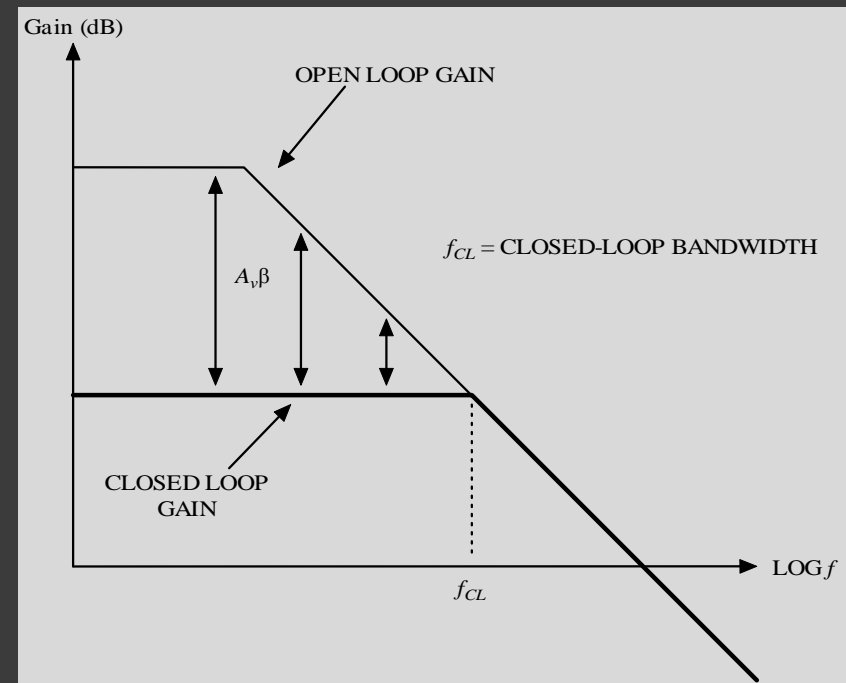
$$\frac{V_o}{V_i} = A_{cl} = \frac{1}{\beta}$$



Negative Feedback “fixes” amplifier problems

- ⊙ Stabilizes the amplifier voltage gain to $\approx 1/\beta$
 - Circuit gain A_{cl} is nearly independent of amplifier gain A_v
- ⊙ Improves input impedance by $(1+A_v\beta)$
 - Decreases loading on upstream amplifiers
- ⊙ Improves output impedance by $(1+A_v\beta)^{-1}$
 - Decreases effect of downstream loads
- ⊙ Increases amplifier bandwidth by decoupling bandwidth from open loop amplifier gain
- ⊙ Improves distortion by $(1+A_v\beta)^{-1}$
 - Improved the quality of transmitted “sound”
- ⊙ *Keep in mind that “ideally” $A_v \rightarrow \infty$, so the benefits are huge*

...But it also caused problems

- ⦿ High open loop gain amplifiers had a tendency to oscillate when the loop was closed
 - *Harry Nyquist* (Bell Labs) established the Nyquist Stability Criterion in 1932...before Black conceived negative feedback...and it applied to open- and closed-loop systems
- ⦿ Analysis of the feedback loop was tedious
 - Lots of multiplication and division and algebra
 - Engineers didn't have calculators or computers until the 70's
- ⦿ *H.W Bode* (Bell Labs) developed a graphical analysis system for feedback stability analysis in 1945 – Bode Plots!
 - Simple analysis because you could “see” the problem
 - Opened the field to more engineers by reducing the specialization required

Gain stabilization example

$$\frac{V_o}{V_i} = \frac{A_v}{1 + A_v\beta}$$

- ⊙ Let $A_v = 20,000$ and $\beta = 0.01$ for an ideal gain of 100
 - $A_{cl}(actual) = 99.502$ or 39.957 dB
- ⊙ Conditions change and A_v drops to $5,000$
 - $A_{cl}(actual) = 98.039$ or 39.828 dB
- ⊙ A 4.9 dB (4x) change in open loop gain and virtually no change in closed loop gain (or bandwidth)
 - 0.129 dB change in gain – you won't notice this
- ⊙ Modern Op Amps have gains of 10^5 to 10^7
 - This reduces the gain error even further


And so the Operational Amplifier was born...but there was still a long way to go

- Still a lot of room for progress

- Open loop gain has improved from ~60 dB to as much as 140 dB
- Differential inputs came later
- Tubes → transistors → integrated circuits
- The cost went from \$1000's to < \$0.50

- But could solve cool problems

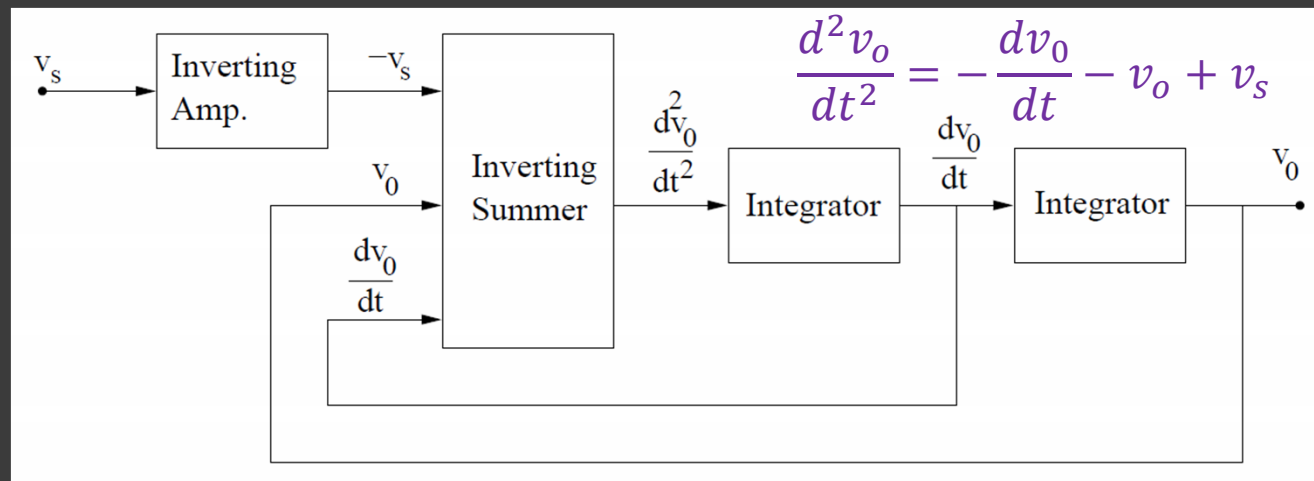- “Operational” – could be used to implement mathematical operations
- Advanced analog computing from mechanical to electronic devices




Current state-of-the-art

- ◎ It is hard to beat the performance of a modern Op Amp
 - Audiophiles will disagree
 - Op Amps can be combined with discrete components to make an improved “composite amplifier”, but this is becoming less common
 - Exceptions are RF, high-power/drive, and some low noise applications
- ◎ Drivers and Trends
 - Portable electronics – Low-power, low-voltage, small footprint, single supply, rail-to-rail
 - Higher integration on chip (auto-zero DAC's, feedback networks)
 - Low-noise, high-bandwidth, high precision
 - *Currently the lowest noise Op Amp has less noise than a 50Ω resistor*
- ◎ Analog has seen a resurgence over the past 20 years

Ideal Op Amps

Ideal Op Amp Assumptions

- ⦿ Infinite open-loop gain (A_v)
 - Voltage between inputs must be zero
- ⦿ Zero offset voltage (V_{os})
 - $V_{OUT} = 0$ when $V_{IN} = 0$
- ⦿ Zero input bias current (I_{bias}^+ , I_{bias}^-)
 - Allows us to easily apply Kirchhoff's Current Law to feedback network
- ⦿ Zero output impedance and infinite input impedance
 - Keeps the analysis simple
- ⦿ Infinite small-signal and large signal bandwidth
 - Infinite slew rate
- ⦿ Infinite output drive and no voltage rails
 - No limits

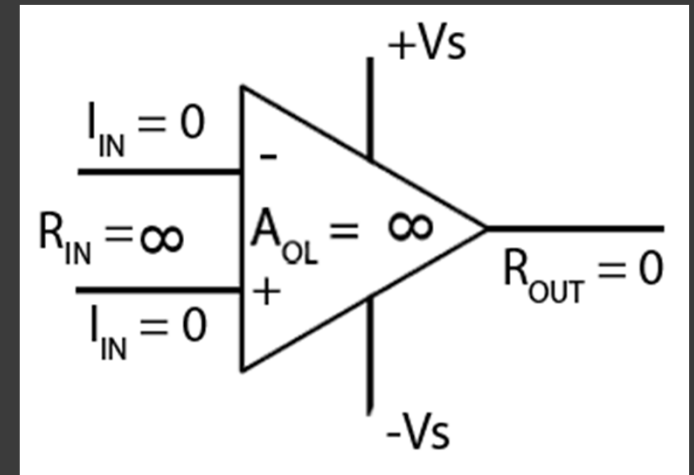

The cake is a lie...

- ◎ **Every single ideal Op Amp assumption is a lie**
 - You will eventually get burned by these the assumptions
 - Assuming you do any “real” design
- ◎ The assumptions make analysis easy
 - Ohm’s Law, KCL, and Superposition are your friends
 - If your circuit doesn’t work with ideal assumptions, it won’t work with a real Op Amp
- ◎ A given Op Amp can approach one or more of these idealities
 - Design is always a series of trade-offs
 - Pick the right amplifier for the application (*‘741’s and ‘324’s suck*)
- ◎ The trick to being a good designer is...
 - ...to know when non-ideal behavior matters
 - ...to know which non-ideal behavior matters in your application
 - ...not to over-specify a component


Inverting Amplifier

- Use KCL and ideal assumptions to compute amplifier gain
 - No voltage across input terminals (infinite gain → virtual ground)
 - No current flowing into input terminals






$$\frac{V_{IN} - 0}{R_g} + \frac{V_{OUT} - 0}{R_f} = 0$$

$$\frac{V_{OUT}}{R_f} = -\frac{V_{IN}}{R_g}$$
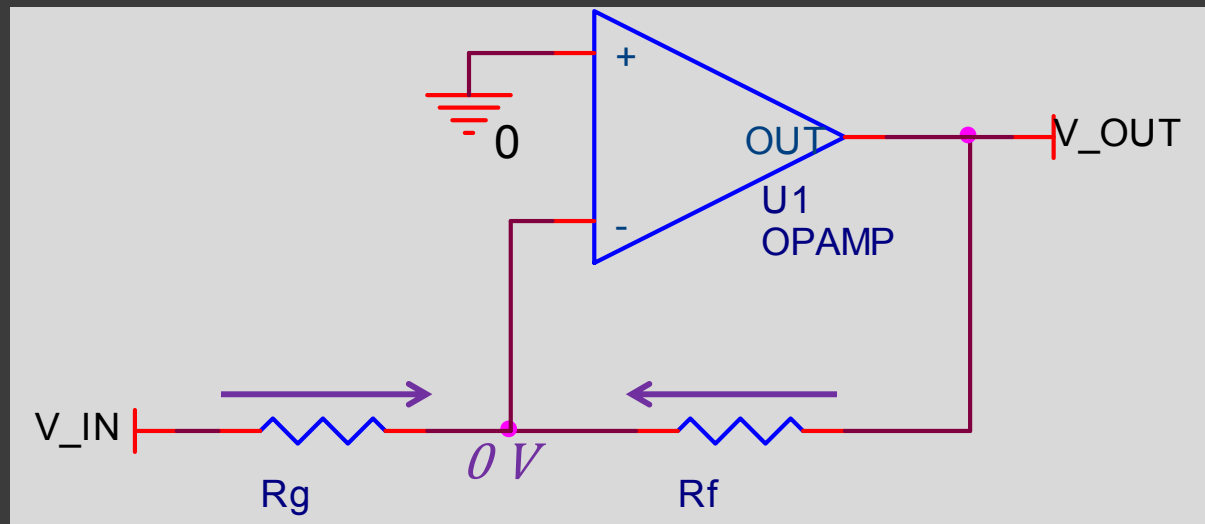
$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_f}{R_g}$$



These are all the same amplifier!

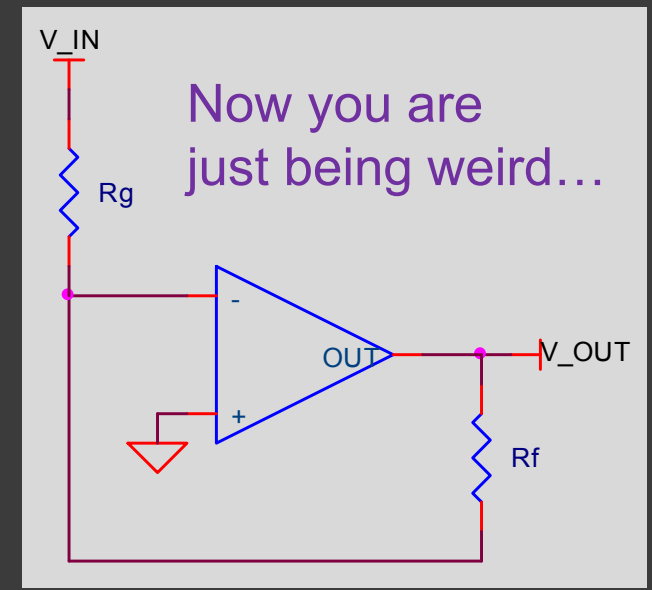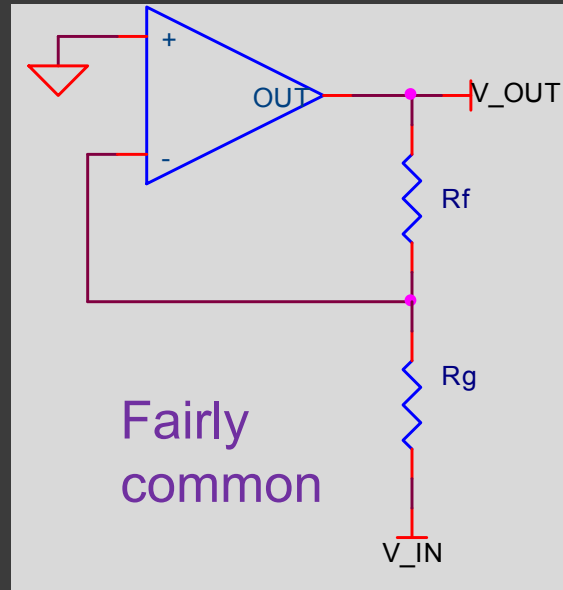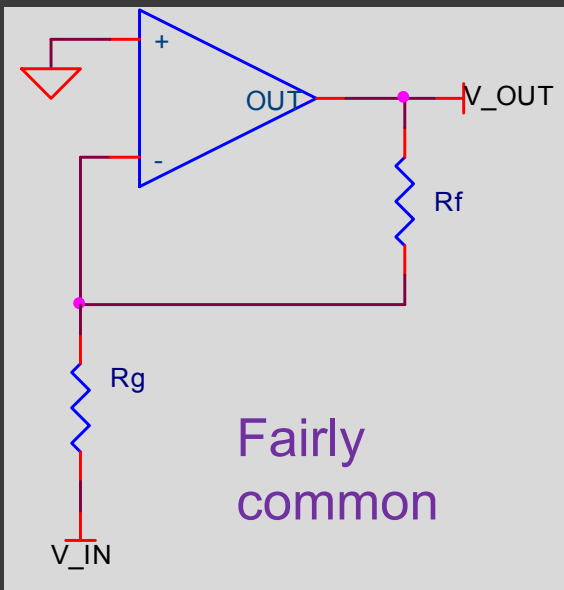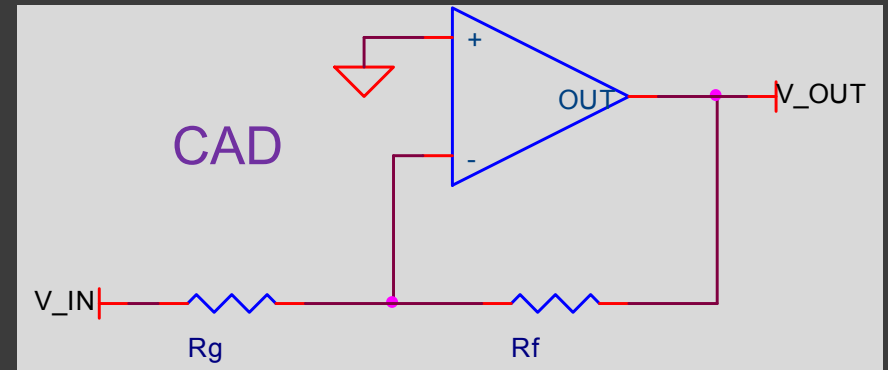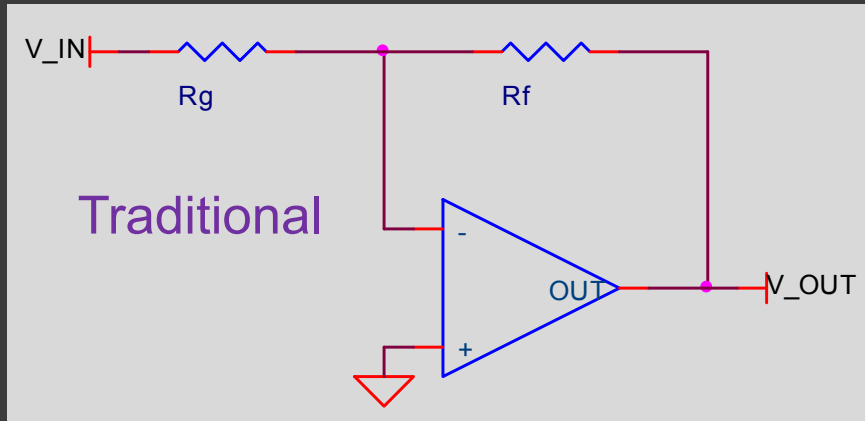

Don't let how the circuit is drawn confuse you!


Computing β

- Compute portion V_{OUT} “fed back” to the inverting input, V_{INV}
 - Ground V_{IN}
 - Use superposition
 - Resistive feedback is just a voltage divider
 - You should have this equation memorized

$$V_{INV} = \frac{R_g}{R_g + R_f} V_{OUT}$$

$$\frac{V_{INV}}{V_{OUT}} = \frac{R_g}{R_g + R_f}$$

$$\beta = \frac{R_g}{R_g + R_f}$$

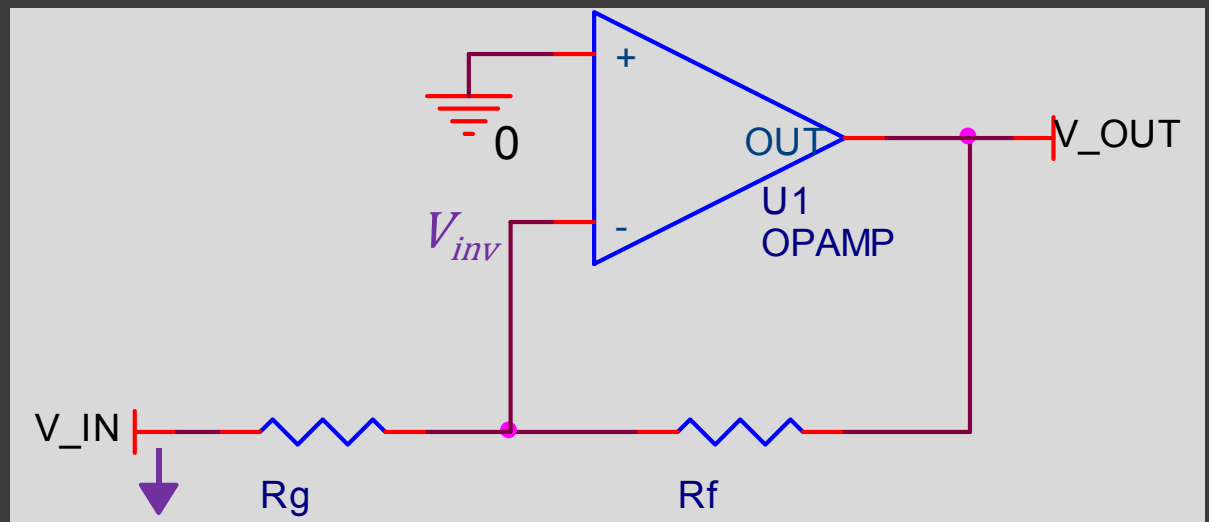


Non-Inverting Amplifier

- Use KCL and ideal assumptions to compute amplifier gain
 - No voltage across input terminals (infinite gain \rightarrow virtual ground)
 - No current flowing into input terminals

$$\frac{0 - V_{IN}}{R_g} + \frac{V_{OUT} - V_{in}}{R_f} = 0$$

$$\frac{V_{OUT}}{R_f} = \frac{V_{IN}}{R_g} + \frac{V_{IN}}{R_f}$$

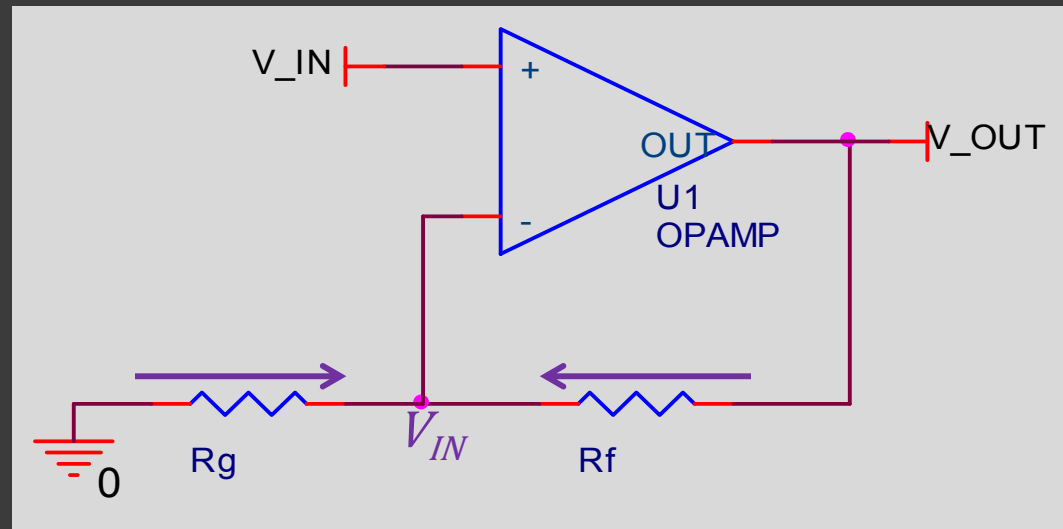
$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_f}{R_g}$$



Non-Inverting Amplifier (Special Case)

- Take the non-inverting amplifier and let
 - $R_f \rightarrow 0$ and $R_g \rightarrow \infty$
- Kind of hard to apply KCL since all currents are zero!
- Recall: no voltage between the input terminals
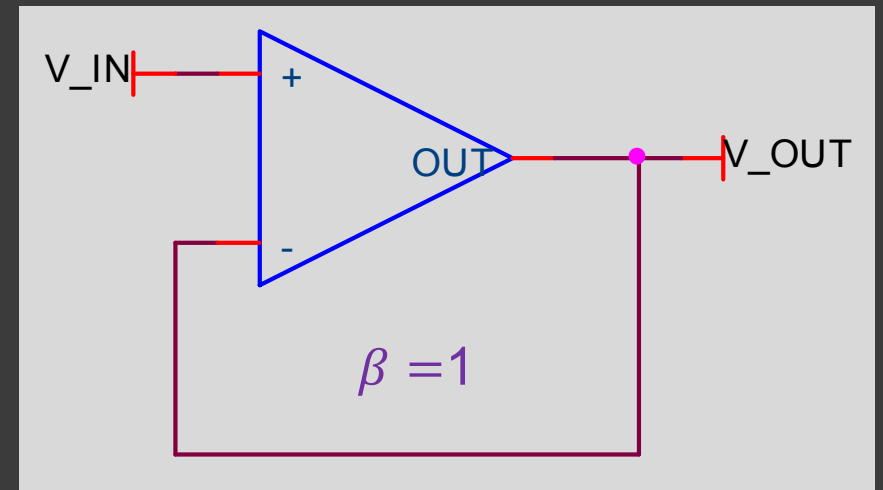
$$V_{OUT} = V_{IN} \quad \frac{V_{OUT}}{V_{IN}} = 1$$




- Called a unity-gain follower or “buffer”
- What purpose does it serve since *nothing* changes?
 - $Z_{IN} \sim \infty$ and $Z_{OUT} \sim 0$
 - “Buffers” a source from a load by providing current gain

Difference Amplifier


- Combine KCL, voltage divider equation, and superposition to computer amplifier gain
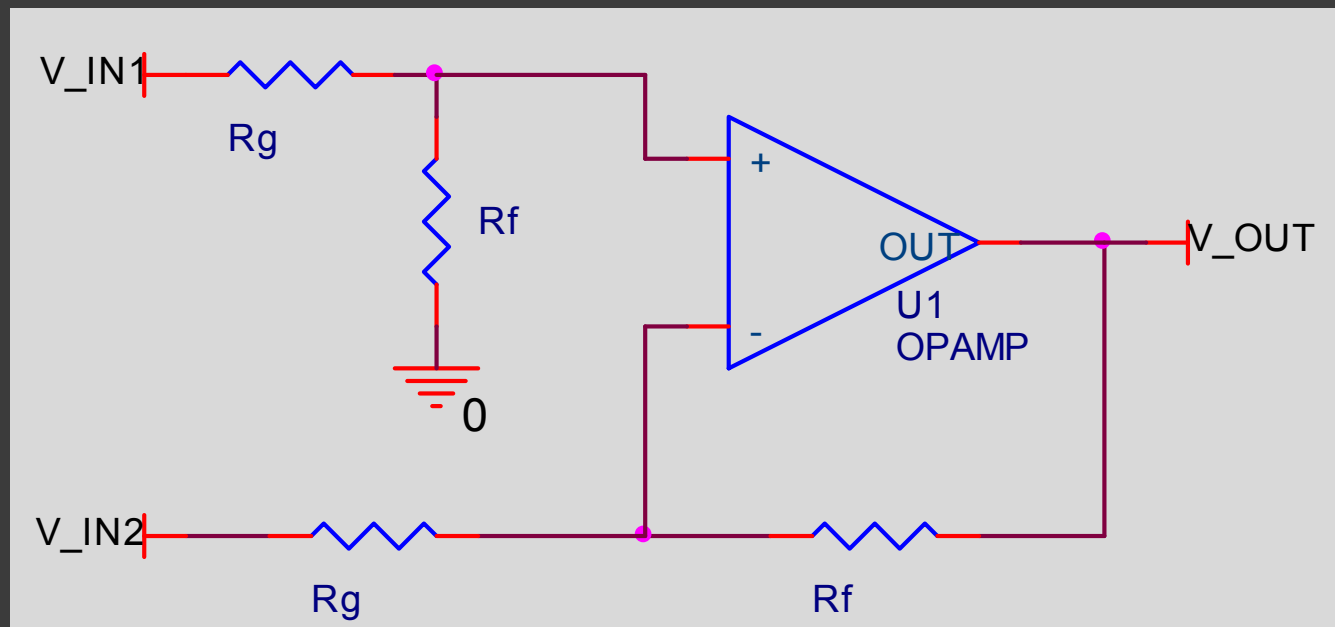
$$V_{OUT} = \frac{R_f}{R_g} (V_{IN1} - V_{IN2})$$




Inverting Summing Amplifier
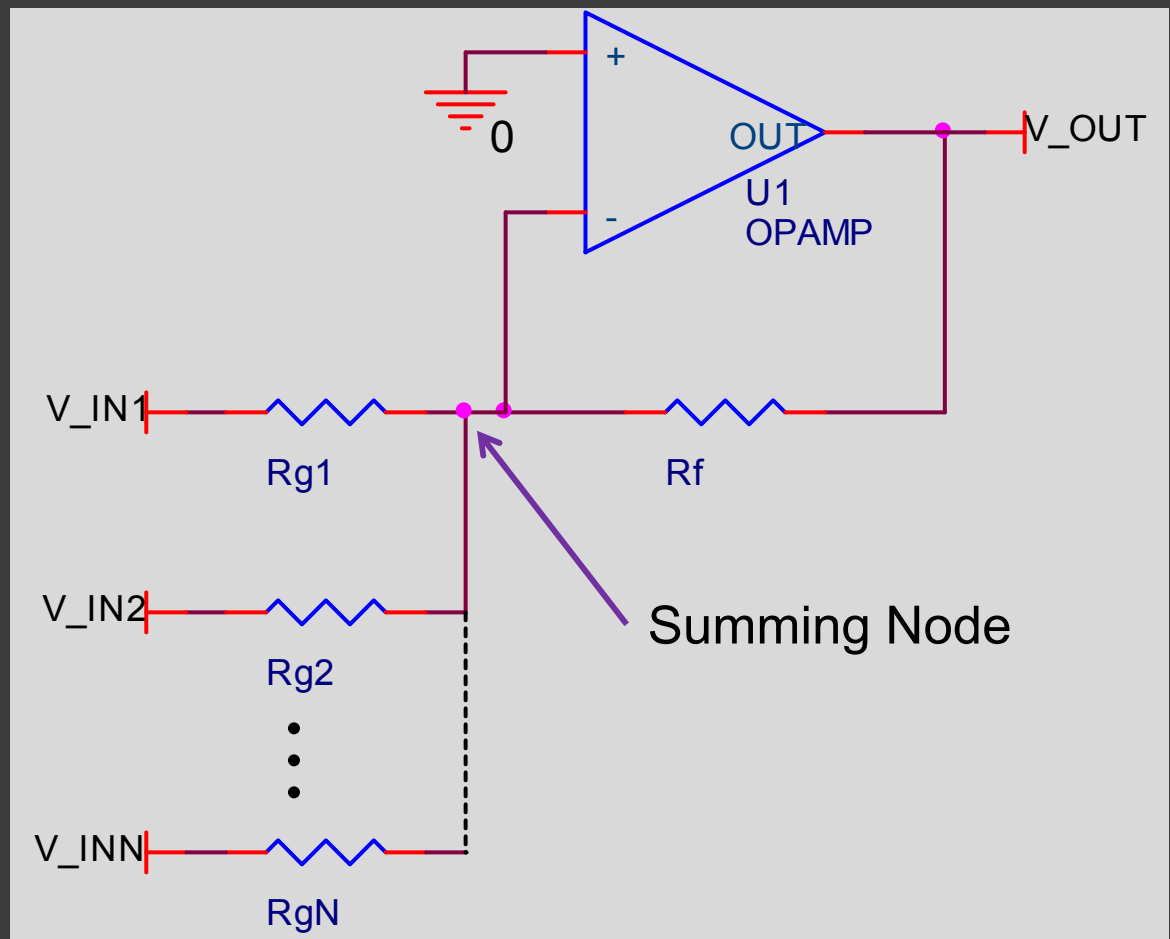
$$V_{OUT} = -\frac{R_f}{R_g} (V_{IN1} + V_{IN2} + \dots + V_{INN})$$



Non-Inverting Summing Amplifier
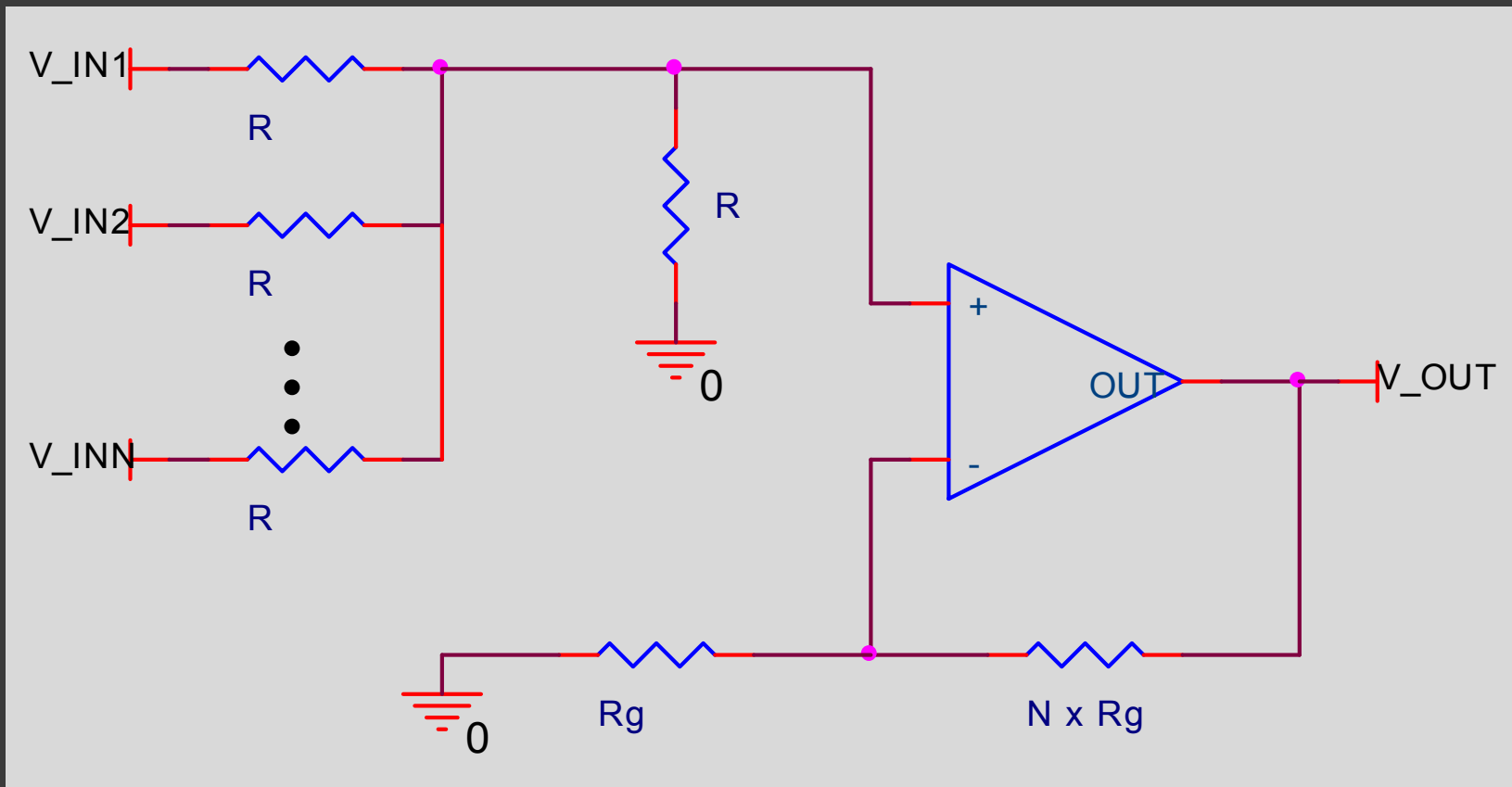
$$V_{OUT} = (V_{IN1} + V_{IN2} + \dots + V_{INN})$$



Integrating Amplifier


$$\frac{v_{in} - 0}{R_g} + i_c = 0$$

$$\frac{v_{in}}{R_g} = -C_1 \frac{dv_c}{dt}$$

$$\int_0^t \frac{v_{in}}{R_g} dt = - \int_0^t C_1 \frac{dv_c}{dt} dt$$

(note that $v_{out} = v_c$)

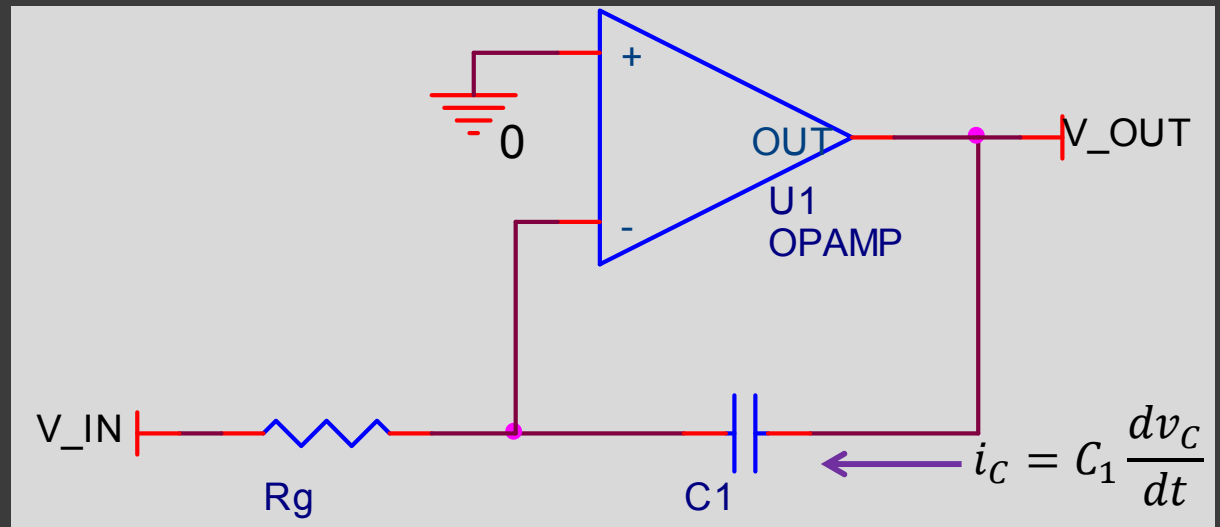
$$v_{out} = - \frac{1}{R_g C_1} \int_0^t v_{in} dt$$



Note: watch out for the initial conditions on the capacitor

Differentiating Amplifier


$$v_o = -R_f C_1 \frac{dv_{in}}{dt}$$

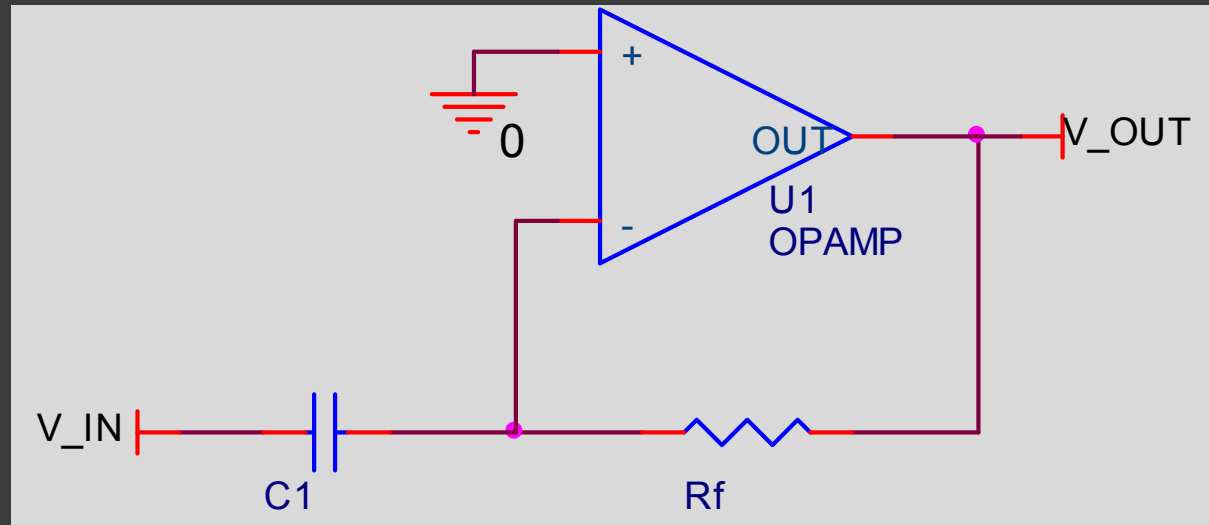


Caution: This circuit is inherently unstable

Bridge Driver


$$v_{OUT} = 2 \frac{R_f}{R_g} v_{IN}$$

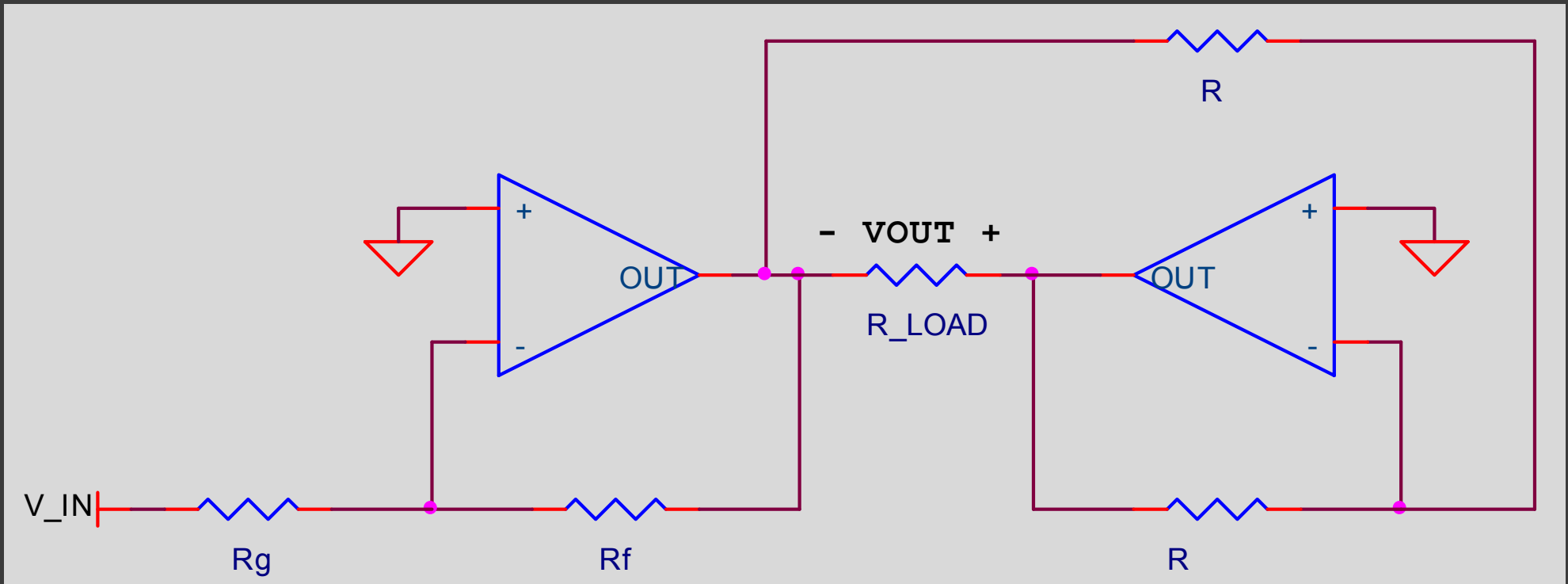

Second-Order Lowpass Active Filters

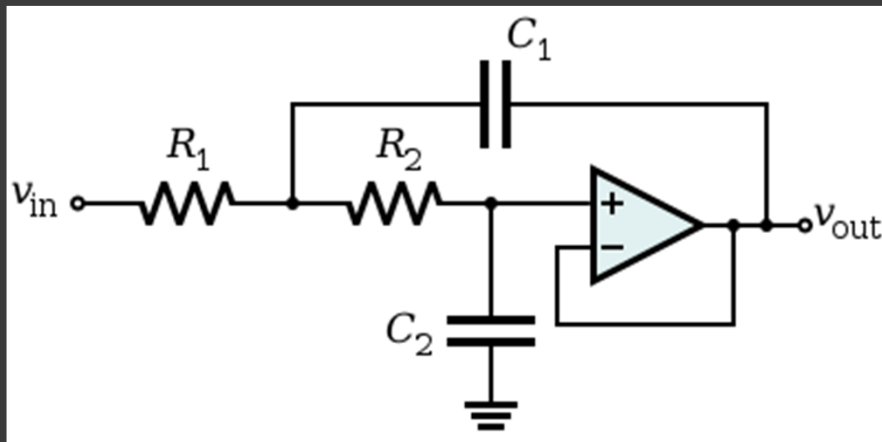

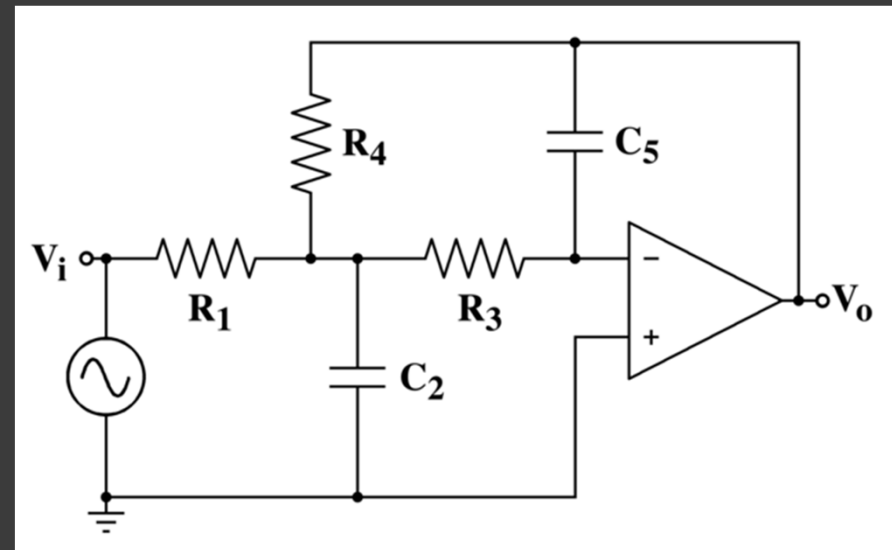Sallen-Key Topology
(non-inverting)
(*some problems*)
(very common)



MFB Topology
(inverting)
(better imho)
(less common)

Resources

- ◎ “*Understanding Basic Analog – Ideal Op Amps*”, Ron Mancini, Application Report SLAA068A, Texas Instruments, April 2000
 - <http://www.ti.com/lit/an/slaa068a/slaa068a.pdf>
- ◎ “*Op Amps for Everyone*” Ron Mancini, SLOD006B, Texas Instruments, August 2002,
 - Good introduction in Chapters 1-3
 - <http://www.ti.com/lit/an/slod006b/slod006b.pdf>
- ◎ “*EEVblog #600 OpAmps Explained*”
 - EEV Blog has some very good videos if you can handle the Aussie accent
 - <http://www.youtube.com/watch?v=7FYHt5XviKc>
- ◎ “*Technote 6 – Opamp Definitions*” and “*Technote 7 – Using Op Amps Successfully*”
 - <http://www.k-state.edu/ksuedl/publications.htm>
 - Courtesy of yours truly

Questions?